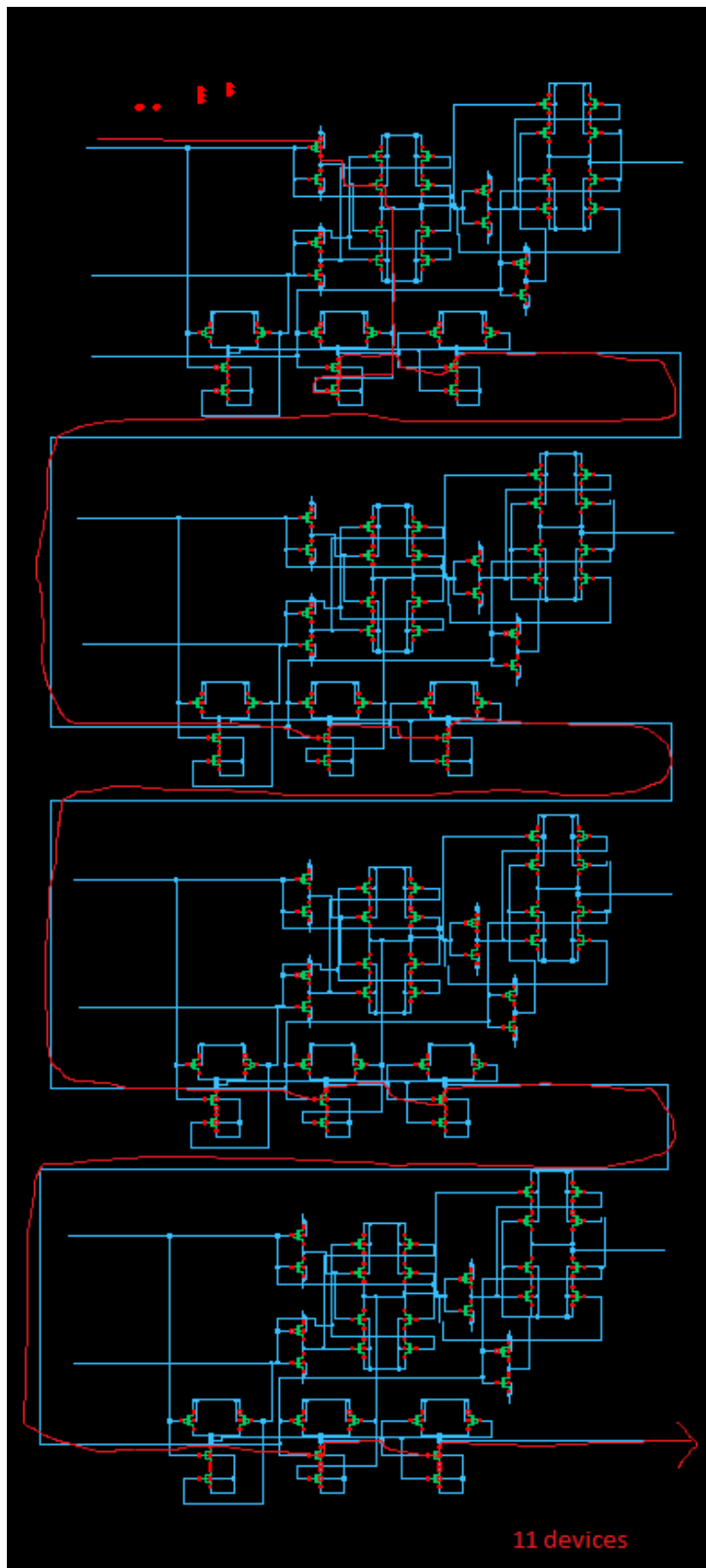


# **Lab 9: Optimization using Logical Effort**

Alex Anderson

ECEN 714-603

First, the critical path was determined from the 4-bit adder circuit:



From this, there are 9 stages (8 NAND and 1 XOR). The calculations of the logical effort are below:

$$(2) G = \prod g_i$$

$$g_{xor} = \frac{C_{in}}{C_{in}} = \frac{8}{3}$$

$$g_{and} = \frac{C_{in}}{C_{in,inv}} = \frac{4}{3}$$

$$G = g_{xor} \cdot g_{and}^8 = \frac{8}{3} + \left(\frac{4}{3}\right)^8 = \frac{49}{3} = \underline{26.637}$$

$$H = \frac{C_{out,path}}{C_{in,path}} = \frac{30fF}{6.548fF} = \underline{4.582}$$

$$B = \prod b_i = \left( \frac{C_{xor} + C_{and}}{C_{and}} \right) \cdot \left( \frac{C_{and} + C_{xor}}{C_{xor}} \right)^8$$

$$= \left( \frac{6.548fF + 3.275fF}{3.275fF} \right) \cdot \left( \frac{3.275fF + 6.548fF}{6.548fF} \right)^8$$

$$= \underline{76.934}$$

$$\hat{f} = F^{1/N} = (G \cdot B \cdot H)^{1/9} = (26.637 \cdot 4.582 \cdot 76.934)^{1/9} = \underline{2.763}$$


$$(3) C_{in,nd} = \frac{g_{and} C_{out}}{f} = \frac{\frac{4}{3} \cdot 30fF}{2.763} = 14.477fF$$



$$\frac{14.477fF}{2.519 \text{ fF}/\mu m} = 5.747 \mu m \Rightarrow \boxed{\begin{matrix} W_p = 1.92 \mu m \\ W_n = 0.96 \mu m \end{matrix}} \text{ NAND}$$

$$C_{in,xor} = \frac{g_{xor} C_{out}}{f} = \frac{\frac{8}{3} \cdot 30fF}{2.763} = 28.954fF$$

$$\frac{28.954fF}{5.037 \text{ fF}/\mu m} = 5.748 \mu m \Rightarrow \boxed{\begin{matrix} W_p = 4.311 \mu m \\ W_n = 1.437 \mu m \end{matrix}} \text{ XOR}$$

The design with the updated sizing was tested using the same cases as Lab 5:

 

  

**Table 1: Non-Optimized Results**

<b>Input Case</b>	<b>Power</b>	<b>Sum Delay</b>	<b>Carry Delay</b>
A=0000 B=1111 C=1	204.6uW	S3=1.102nS S2=850ps S1=598.5ps S0=361ps	1.202ns
A=1010 B=0101 C=0	207.1uW	S3=1.157ns S2=907.5ps S1=658.2ps S0=416.7ps	1.176ns
A=1010 B=0101 C=1	204.6uW	S3=1.102ns S2=850.7ps S1=599.1ps S0=358.3ps	1.202ns
A=1100 B=1000 C=0	209.9uW	S3=850.1ps S2=636.5ps S1=602.6ps S0=392.8ps	463.3ps

**Table 2: Optimized Results**

<b>Input Case</b>	<b>Power</b>	<b>Sum Delay</b>	<b>Carry Delay</b>
A=0000 B=1111 C=1	394.7uW	S3=899.4ps S2=659.1ps S1=418.6ps S0=162.3ps	956.5ps
A=1010 B=0101 C=0	392.8uW	S3=918.2ps S2=666.2ps S1=414.5ps S0=150.9ps	1ns
A=1010 B=0101 C=1	394.5uW	S3=899.4ps S2=659.1ps S1=418.6ps S0=162.3ps	956.5ps
A=1100 B=1000 C=0	430.6uW	S3=692.8ps S2=400.3ps S1=436.0ps S0=277.3ps	254.5ps

Overall, the delays improved on average by **18%** while the power consumption increased by **95%**.

**Table 3: Area Comparison**

<b>Design</b>	<b>Approx. Area (um<sup>2</sup>)</b>
Optimized	59.424
Non-Optimized	17.12