Lab 2: Introduction to Cadence Schematic Capture & Simulation

Alex Anderson

UIN: 728001757

ECEN 714-603

Inverter:

 


Figure 1: Inverter Schematic

 


Figure 2: Inverter Layout

 


Figure 3: Inverter Symbol

 


Figure 4: Inverter Extracted View

```
@(#)$CDS: LVS version 6.1.8-64b 08/04/2020 19:19 (cpgsrv11) $
Command line: /opt/coe/cadence/IC618/tools.lnx86/dfII/bin/64bit/LVS -dir /home/ugrads/a/alexd43anderson/ecen714/LVS -l -s -t /home/ug Like matching is enabled.

Net swapping is enabled.

Using terminal names as correspondence points.
Compiling Diva LVS rules...
     Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/layout/netlist
        count
         4
                            terminals
                           pmos
                           nmos
     Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/schematic/netlist
        count
         4
                           nets
                           terminals
                           pmos
                           nmos
    Terminal correspondence points NO N3 GND
     N3
                N1
                            VDD
     N2
     N1
                N2
                           out
Devices in the netlist but not in the rules:
         pcapacitor
Devices in the rules but not in the netlist:
         cap nfet pfet nmos4 pmos4
The net-lists match.
                                  layout schematic
                                     instances
         un-matched
                                     0
                                              0
         rewired
                                     0
                                              0
         size errors
                                     0
                                              0
         pruned
                                              0
          .
active
                                     2
                                              2
         total
```

Figure 5: Inverter LVS Check

NAND2:

 


Figure 6: NAND2 Schematic

 


Figure 7: NAND2 Symbol

 


Figure 8: NAND2 Layout

 


Figure 9: NAND2 Extracted View

```
@(#)$CDS: LVS version 6.1.8-64b 08/04/2020 19:19 (cpgsrv11) $
Command line: /opt/coe/cadence/IC618/tools.lnx86/dfII/bin/64bit/LVS -dir /home/ugrads/a/alexd43anderson/ecen714/LVS -l -s -t /home/ug
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...
    Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/layout/netlist
       count
        5
                         terminals
        2
                         pmos
        2
                         nmos
    Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/schematic/netlist
        6
                         nets
        5
2
2
                         terminals
                         pmos
                         nmos
    Terminal correspondence points
    N4
              N3
                         A
B
    N3
               N5
    N1
              N0
                         GND
    N2
                         OUT
    N5
                         VDD
Devices in the netlist but not in the rules:
        pcapacitor
Devices in the rules but not in the netlist:
        cap nfet pfet nmos4 pmos4
The net-lists match.
                              layout schematic
                                 instances
        un-matched
                                          0
        rewired
                                          0
        size errors
                                 0
                                          0
        pruned
                                 0
                                          0
        .
active
                                 4
                                          4
        total
```

Figure 10: NAND2 LVS Check

XOR2:

 


Figure 11: XOR2 Schematic

 


Figure 12: XOR2 Layout

 


Figure 13: XOR2 Symbol

 


Figure 14: XOR2 Extracted View

```
@(#)$CDS: LVS version 6.1.8-64b 08/04/2020 19:19 (cpgsrv11) $
Command line: /opt/coe/cadence/IC618/tools.lnx86/dfII/bin/64bit/LVS -dir /home/ugrads/a/alexd43anderson/ecen714/LVS -l -s -t /home/ug
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...
    Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/layout/netlist
       count
        11
                         nets
        5
                         terminals
        6
                        pmos
        6
                         nmos
    Net-list summary for /home/ugrads/a/alexd43anderson/ecen714/LVS/schematic/netlist
       count
        11
                         nets
        5
                         terminals
        6
                         pmos
        6
    Terminal correspondence points
    N9
              N3
    N8
              N7
    N6
              Ν1
                         GND
    N7
              NO
                         OUT
    N10
                         VDD
              N5
Devices in the netlist but not in the rules:
        pcapacitor
Devices in the rules but not in the netlist:
        cap nfet pfet nmos4 pmos4
The net-lists match.
                              layout schematic
                                 instances
        un-matched
                                 0
                                         0
        rewired
                                 0
                                         0
        size errors
                                 0
                                         0
        pruned
        .
active
                                 12
                                         12
        total
```

Figure 15: XOR2 LVS Check